
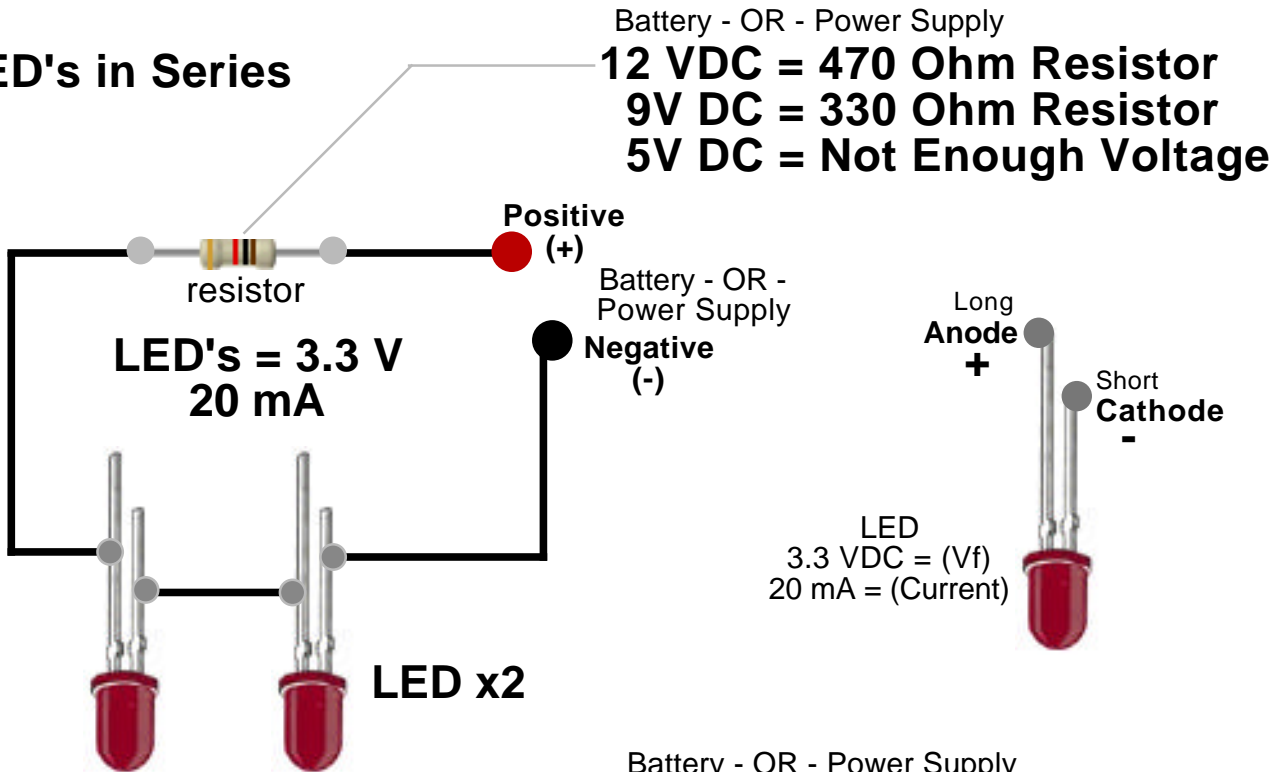


LED's Series / Parallel Setup

LED's in Series

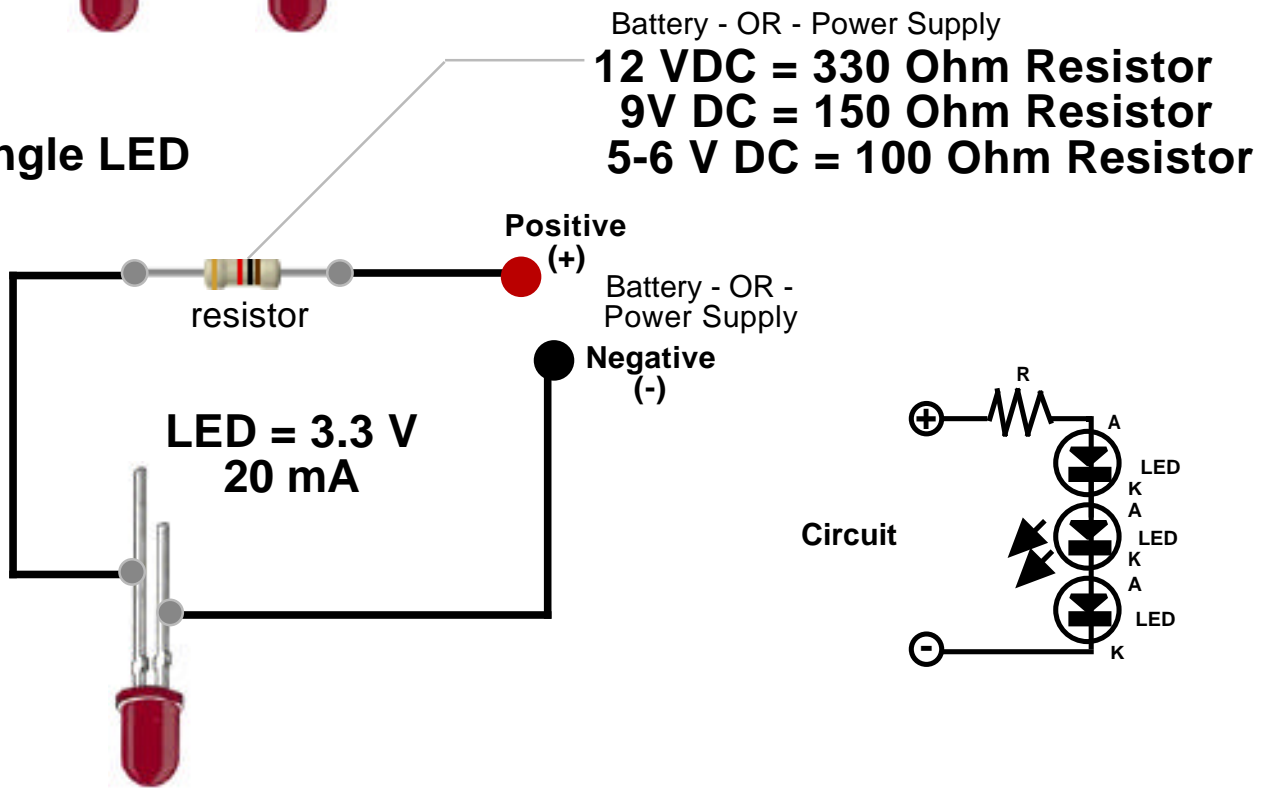

Single LED



Copyright © 2009 Blue Point Engineering, All Rights Reserved


Custom Equipment, Unique Electronic Products

Blue Point Engineering

Phone (303) 651-3794
 www.BPEsolutions.com


LED's Series / Parallel Setup

LED's in Parallel

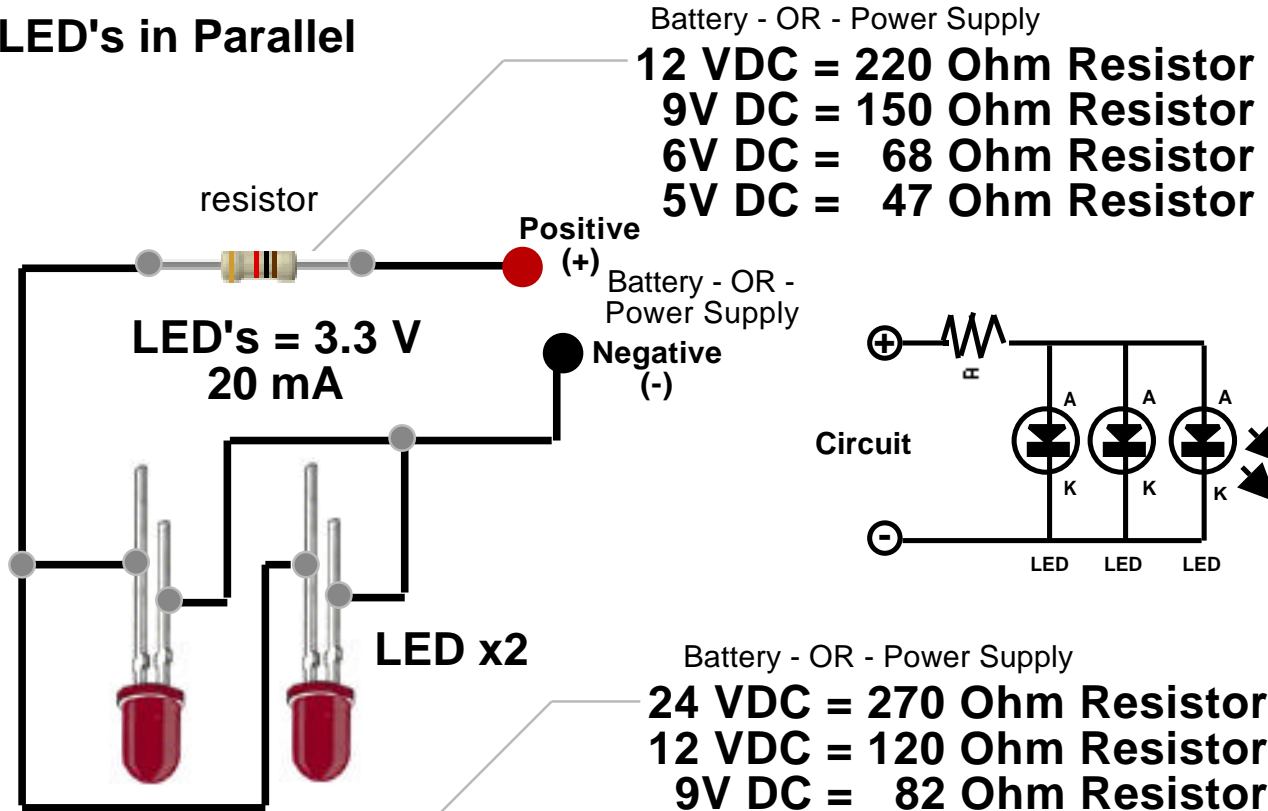

Battery - OR - Power Supply

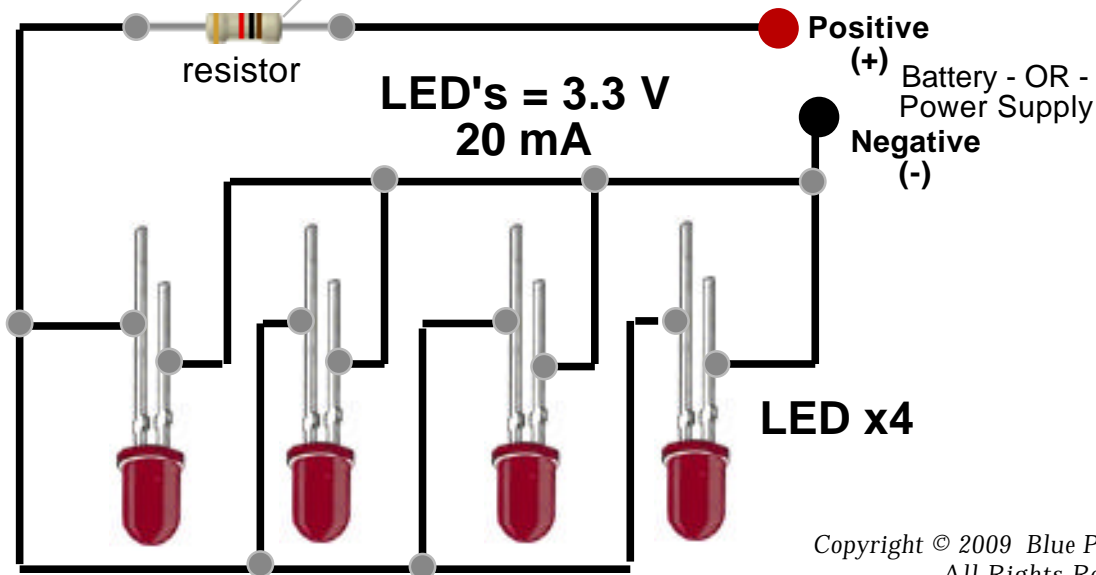24 VDC = 270 Ohm Resistor
12 VDC = 120 Ohm Resistor
9V DC = 82 Ohm Resistor
6V DC = 68 Ohm Resistor
5V DC = 22 Ohm Resistor
4V DC = 10 Ohm Resistor



Copyright © 2009 Blue Point Engineering,
All Rights Reserved

Custom Equipment, Unique Electronic Products


Blue Point Engineering

Phone (303) 651-3794
www.BPEsolutions.com

LED's Series / Parallel Setup


LED's in Parallel

* Best Setup

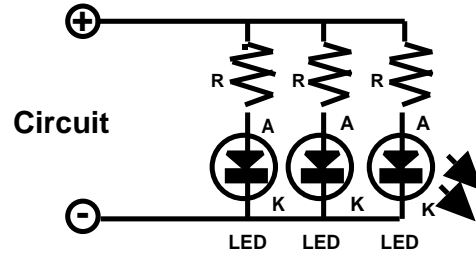

Battery - OR - Power Supply

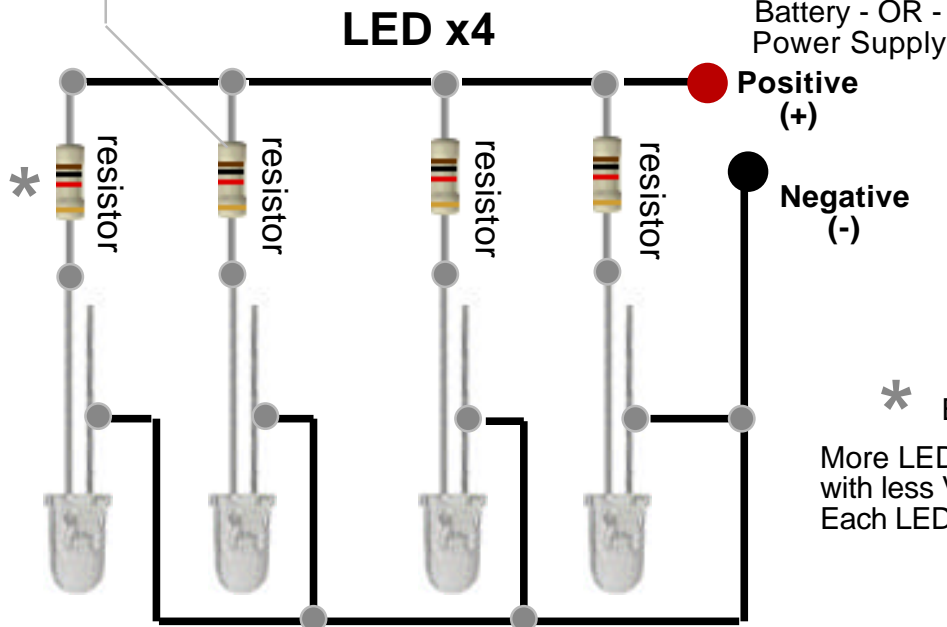24 VDC = 270 Ohm Resistor
 12 VDC = 120 Ohm Resistor
 9V DC = 82 Ohm Resistor
 6V DC = 68 Ohm Resistor
 5V DC = 22 Ohm Resistor
 4V DC = 10 Ohm Resistor



LED's = 3.3 V
 20 mA

Copyright © 2009 Blue Point Engineering, All Rights Reserved

Custom Equipment, Unique Electronic Products

Blue Point Engineering

Phone (303) 651-3794
 www.BPEsolutions.com

Blue Point Engineering Inc.

LED Information

Controller

| LED | Voltage Drop Vf | Foward Current mA | LED Intensity Level mcd |
|--------|-----------------|-------------------|-------------------------|
| White | 3.3 Vdc | 20 mA | 8000 mcd |
| Blue | 3.1 vdc | 20 mA | 6000 mcd |
| Green | 3.3 vdc | 20 mA | 4000 mcd |
| Red | 2.25 Vdc | 20 mA | 8000 mcd |
| Yellow | 1.9 Vdc | 20 mA | 3000 mcd |

Check with LED manufacture to determine actual Vf, mA, values

To calculate resistance. Ohms law is $V=IR$. Solving for R yields $R=V/I$
 V is voltage in volts, I is current in amps, and R is resistance in Ohms.
 V is the difference between the supplied voltage and the required voltage.

Since we're using milliamps instead of amps, we need a multiplication factor of 1000.
 Since we're using the difference in supplied voltage and required LED voltage we need to subtract. The formula becomes $R = (9 \text{ volts} - \text{LED voltage required}) / (\text{current in milliamps}) * 1000$

Once you've calculated the resistance, you will use the closest resistor value you can find.

Example: White LED = **3.3 Vf 30mA** Power Supply- **9Vdc**

$$9\text{Vdc} - 3.3\text{Vdc} / 20\text{mA} \times 1000 = 285$$

Resistor Needed = **330 Ohm 1/4 Watt**

(Nearest Resistor Value (330) Orange/Orange/Brown/Gold)

Calculated resistance value = 285 Ohms



Next standard 10% resistor = 330 Ohm

Power dissipated in LED = 0.114 Watts

Power dissipated in resistor = 0.19 Watts

Each LED should have it's own current limiting series resistor if possible.

Resistor 

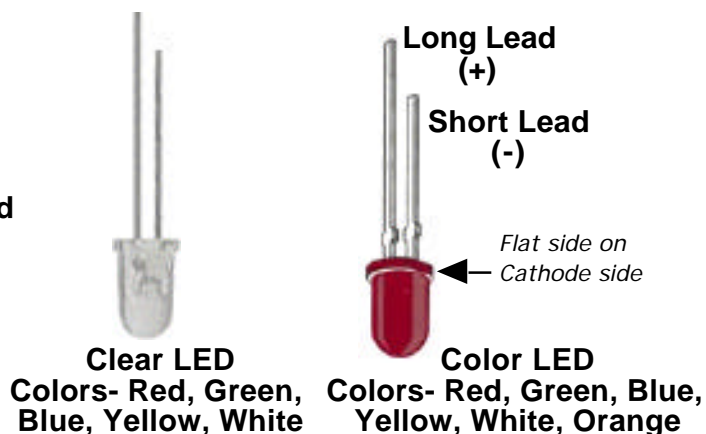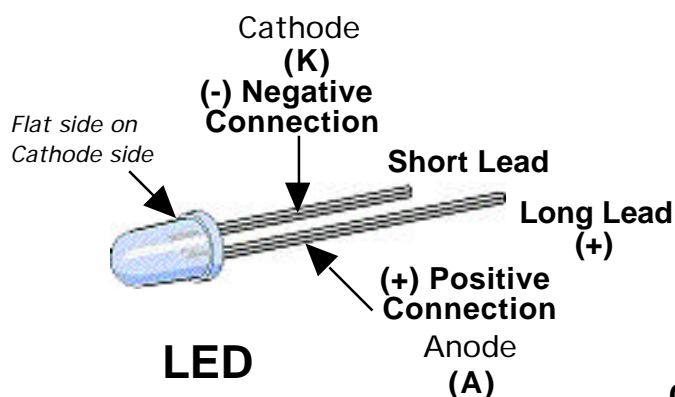

Custom Equipment, Unique Electronic Products

Blue Point Engineering Inc.

Phone (303) 651-3794

www.BPEsolutions.com